
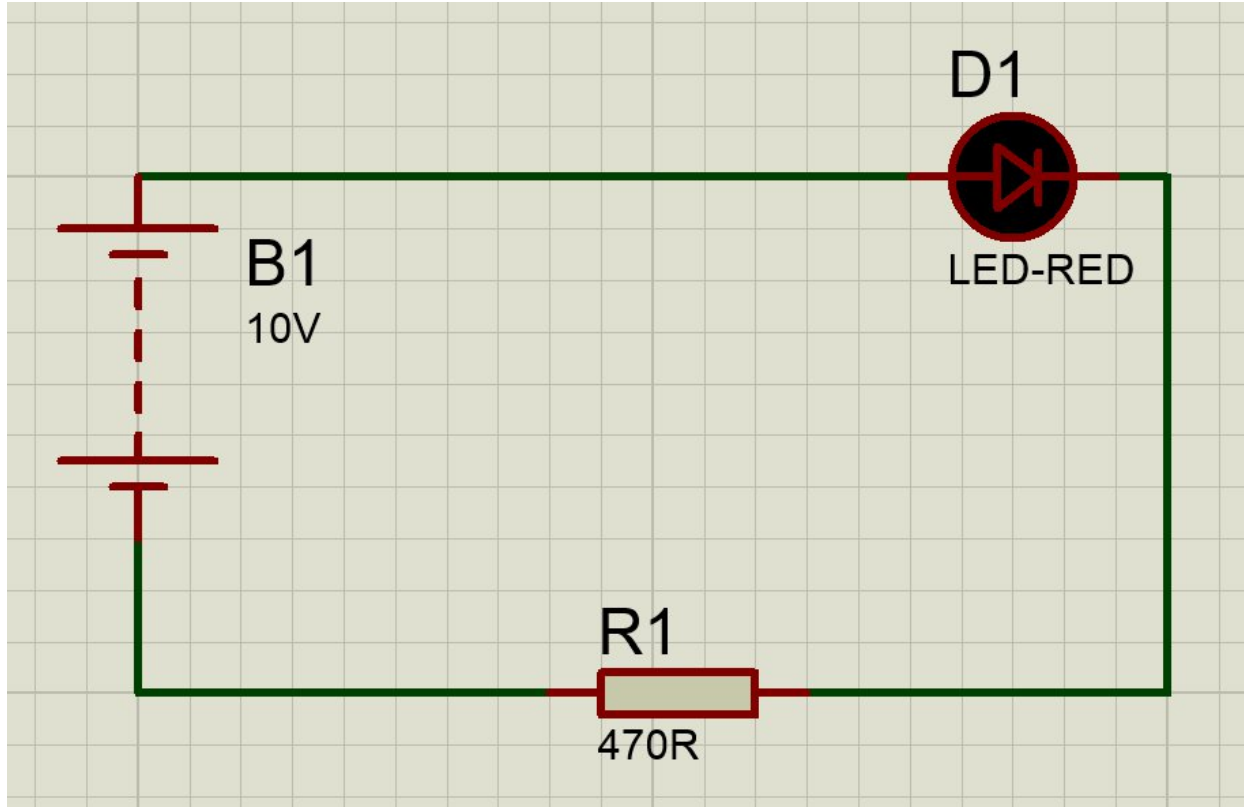


ME 2261 - Embedded Systems Log Book


Task 1

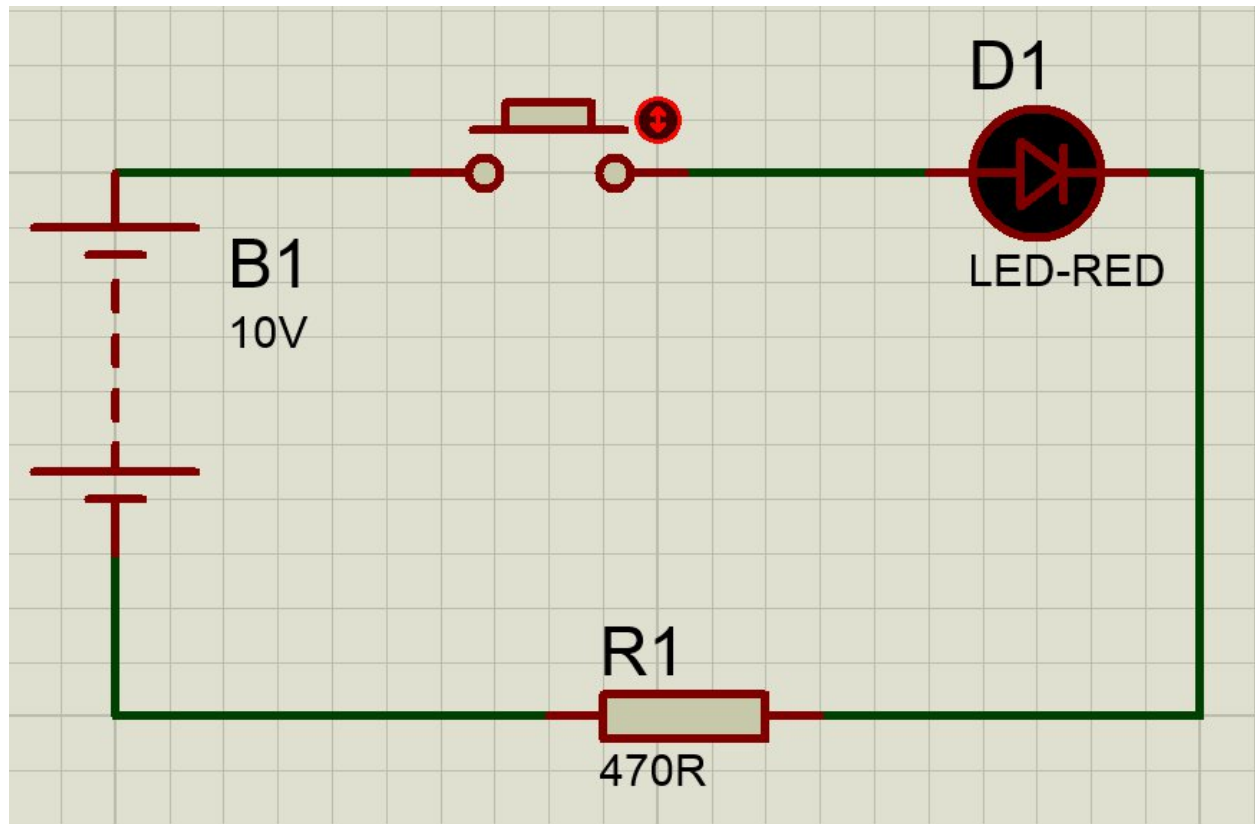


Task 2




Task 3

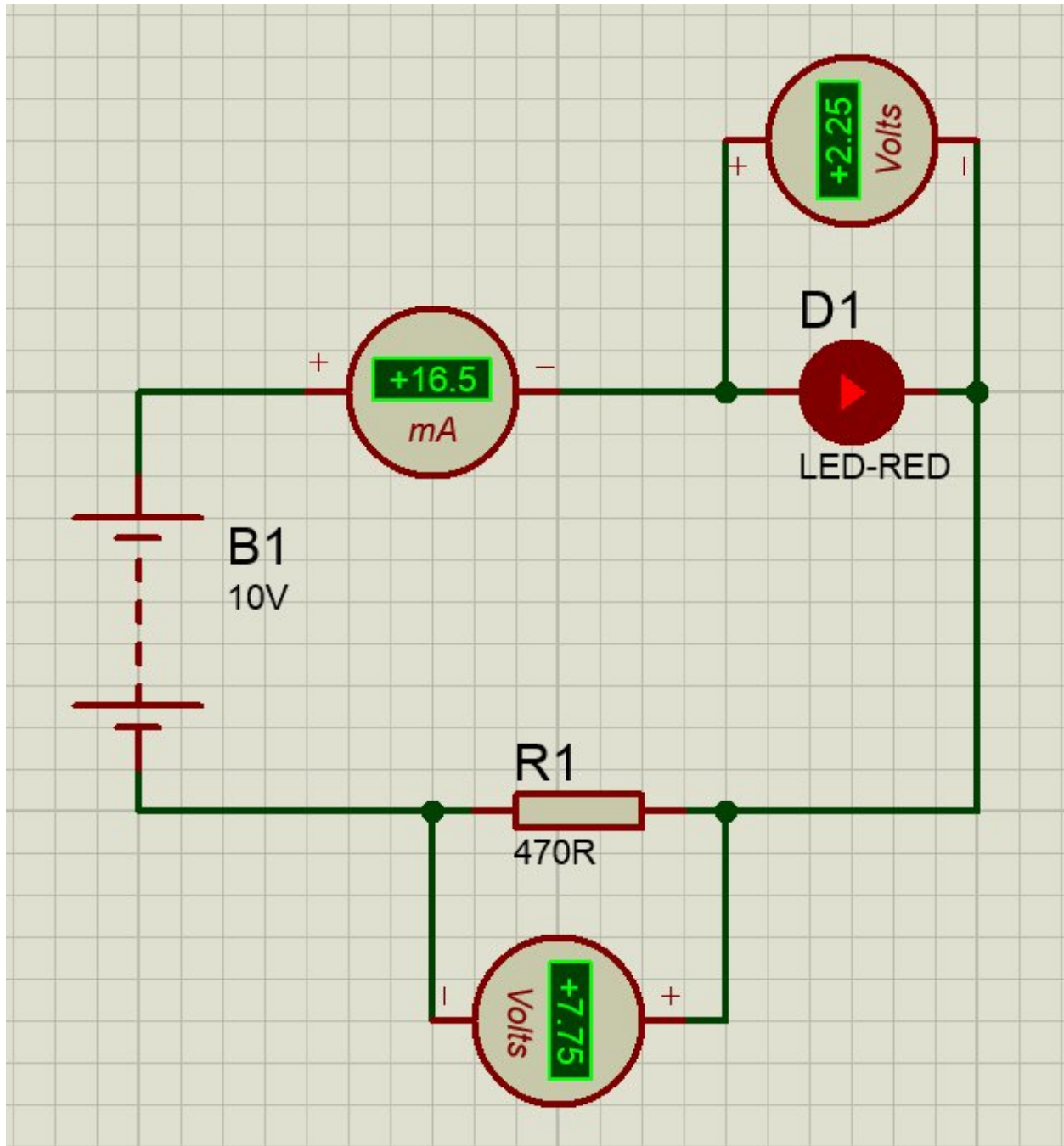


Task 4

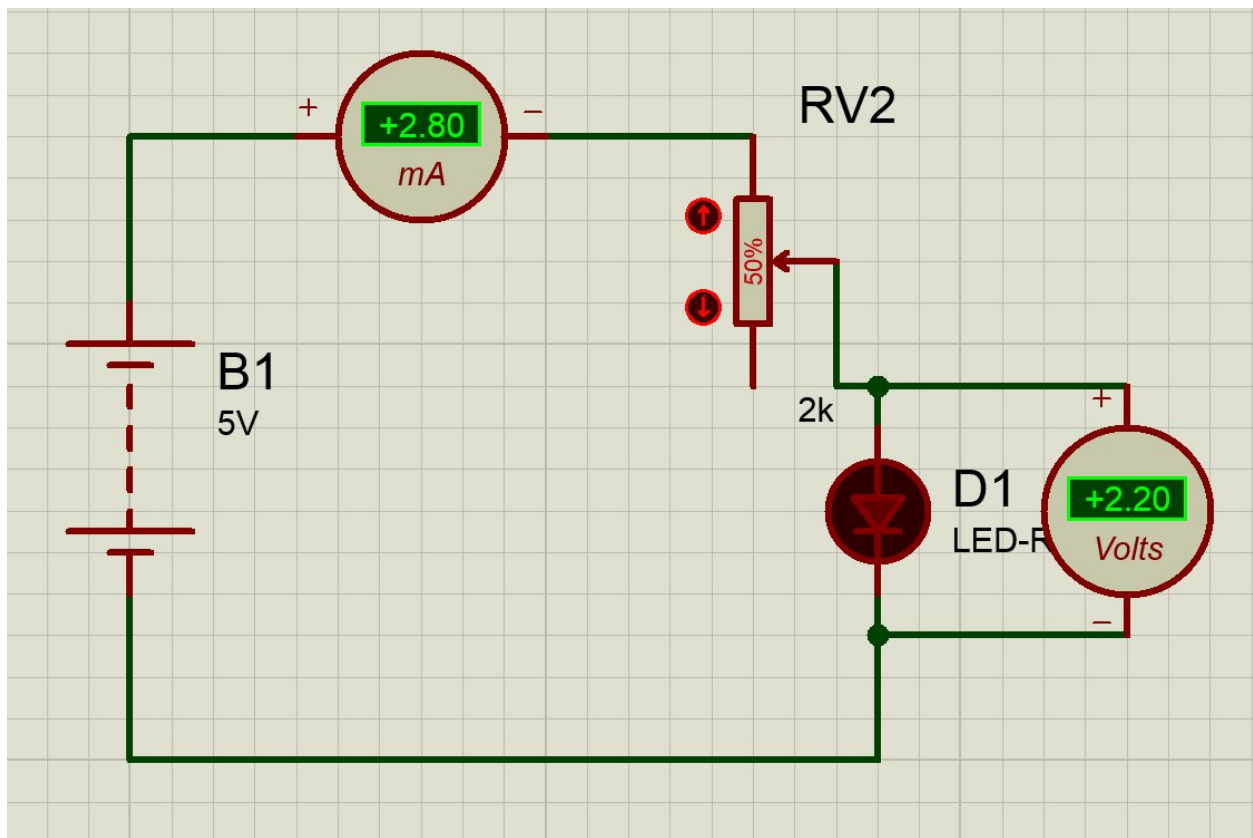


Task 5

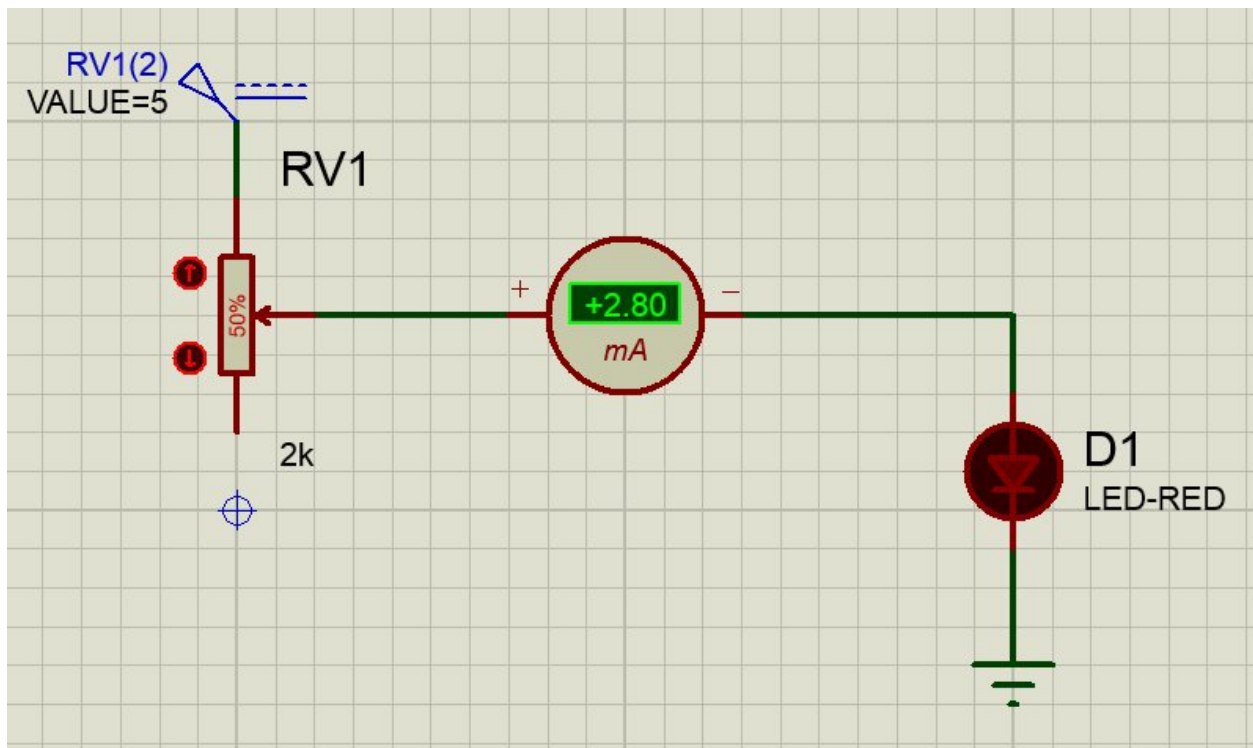

Task 6

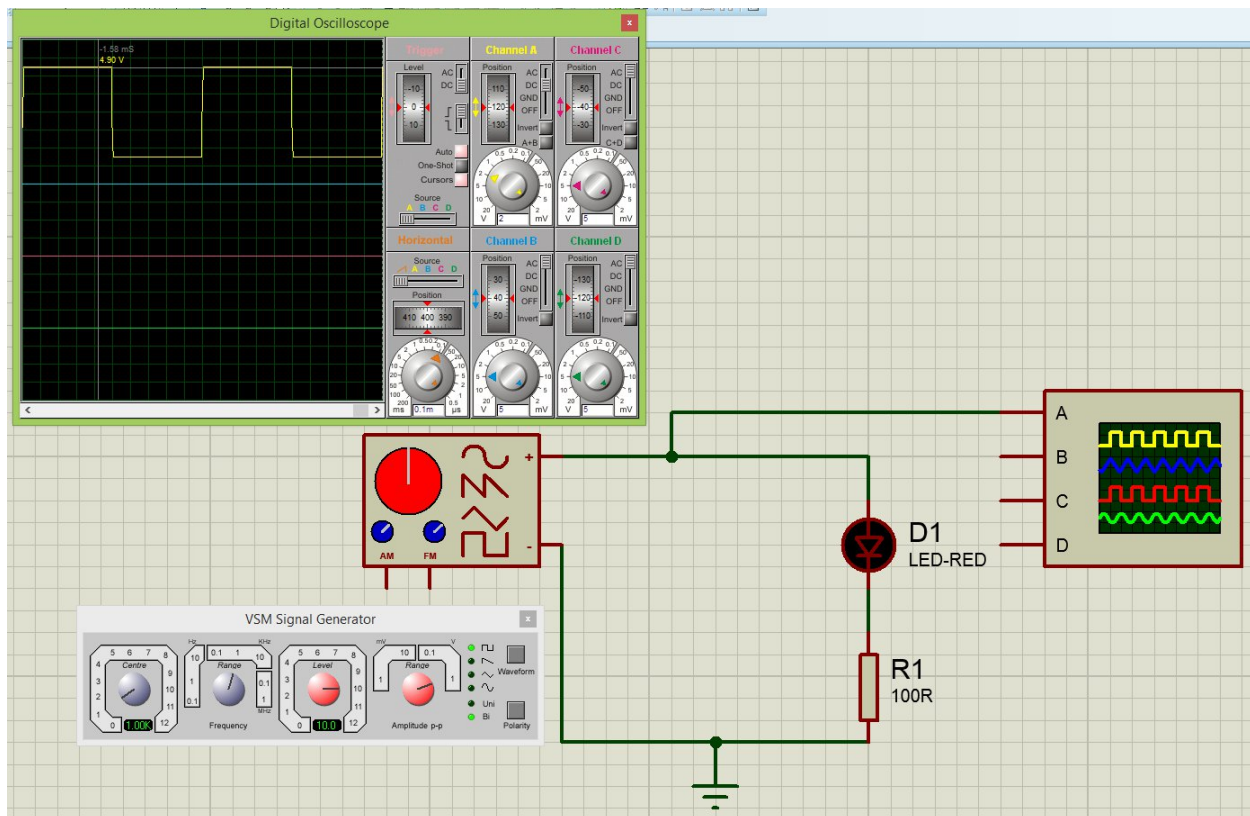


Task 7

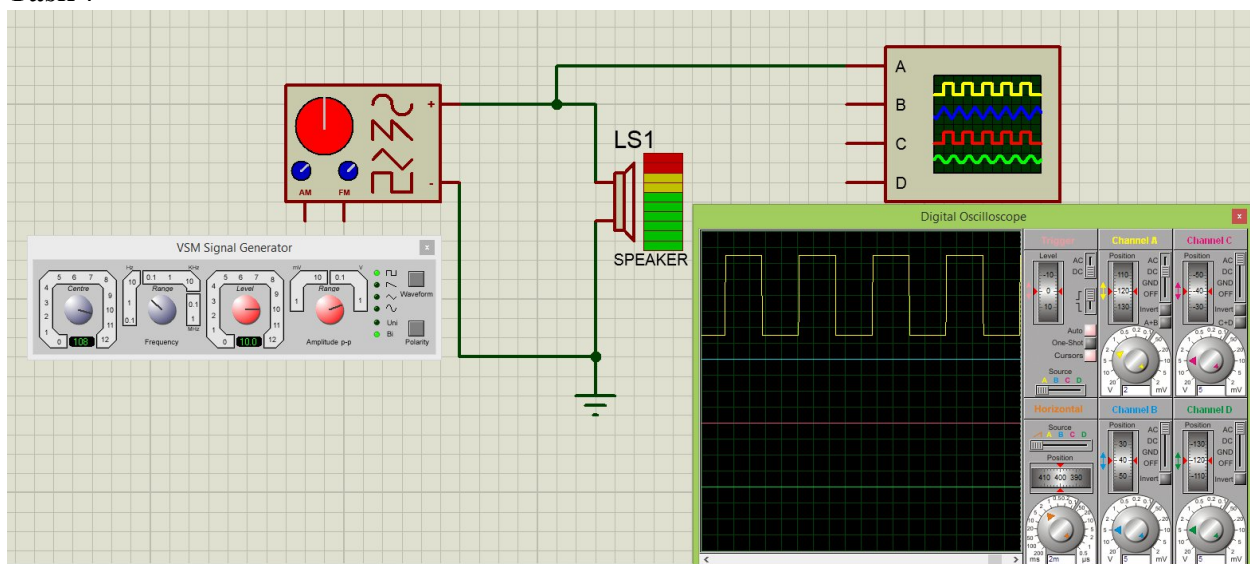


2-input NOT gate


70XX series- 7404 IC

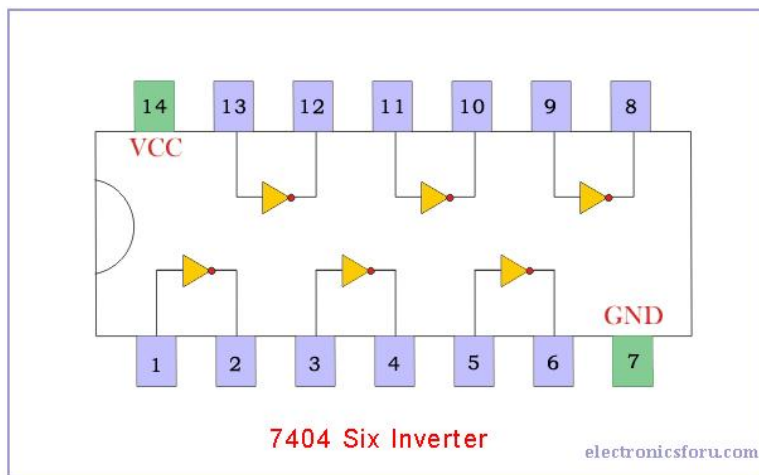

40XX series - 4069 IC

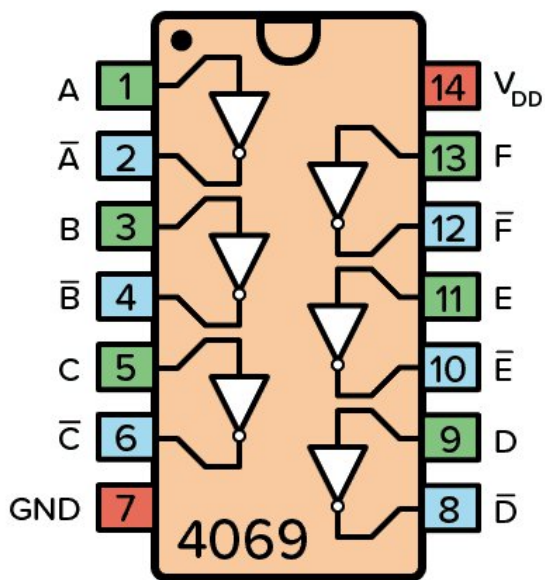


A	F
0	1
1	0

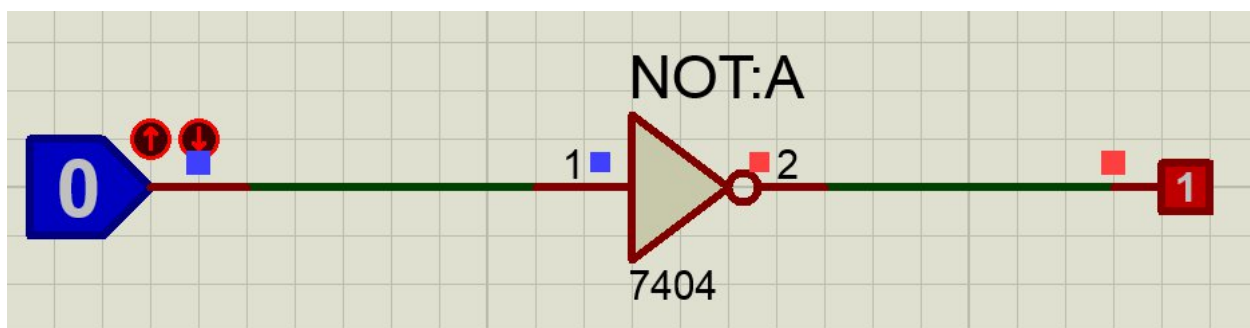

2-input AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


7408 and 4081 IC

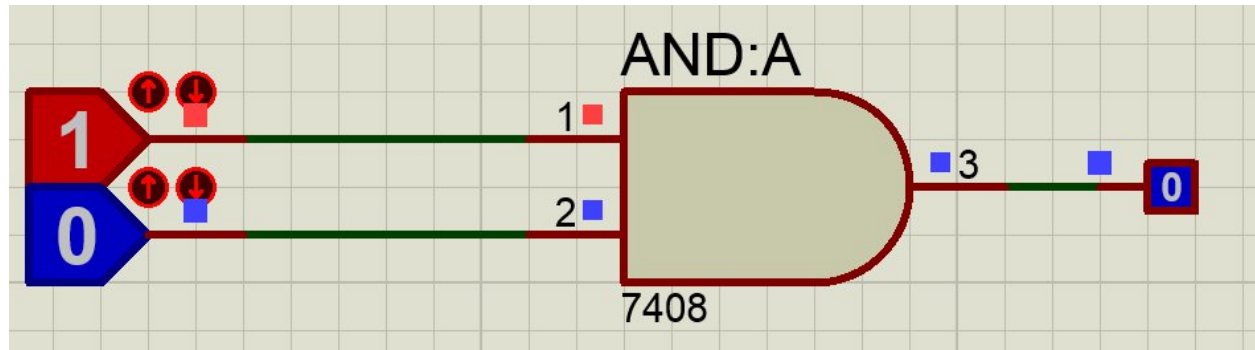

2-input OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1


7432 and 4071 IC

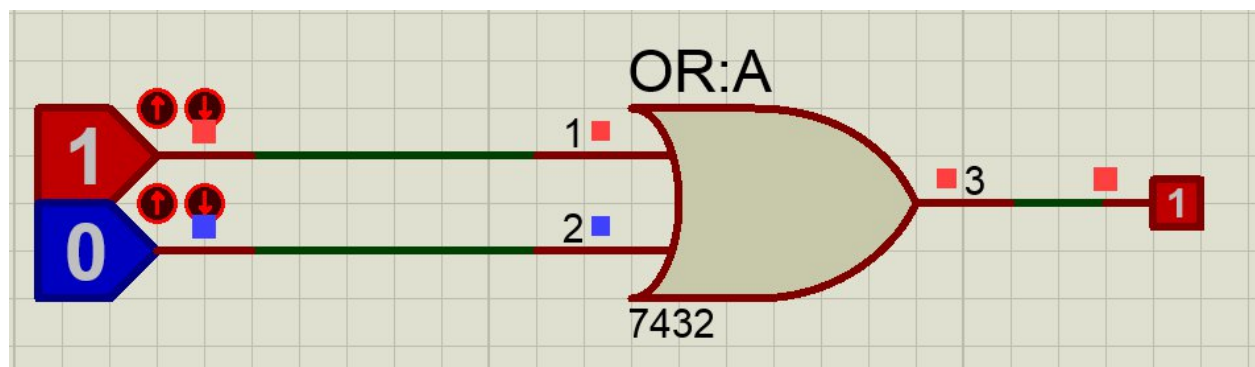

2-input NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


7402 and 4001 IC

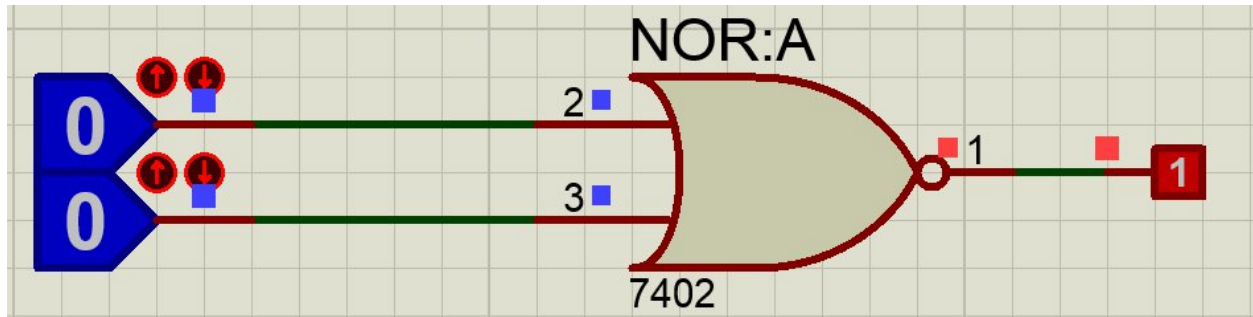

2-input NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


7400 and 4011 IC

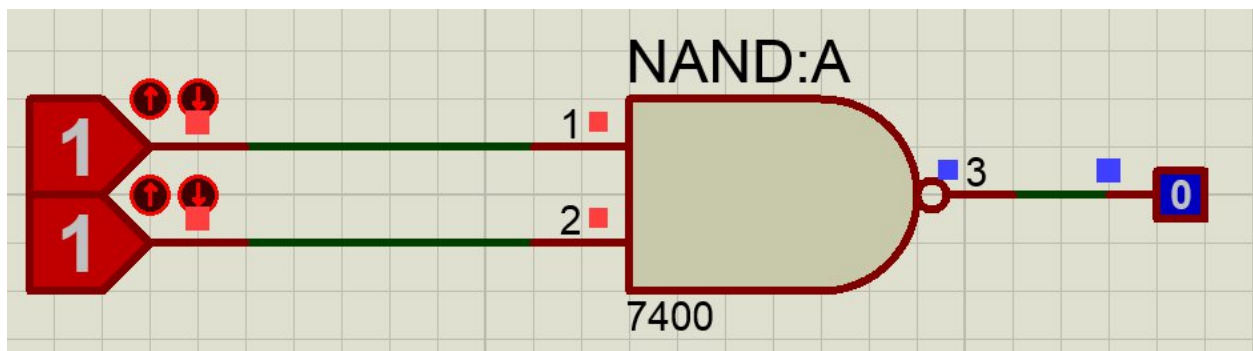

2-input XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

7486 and 4070 IC

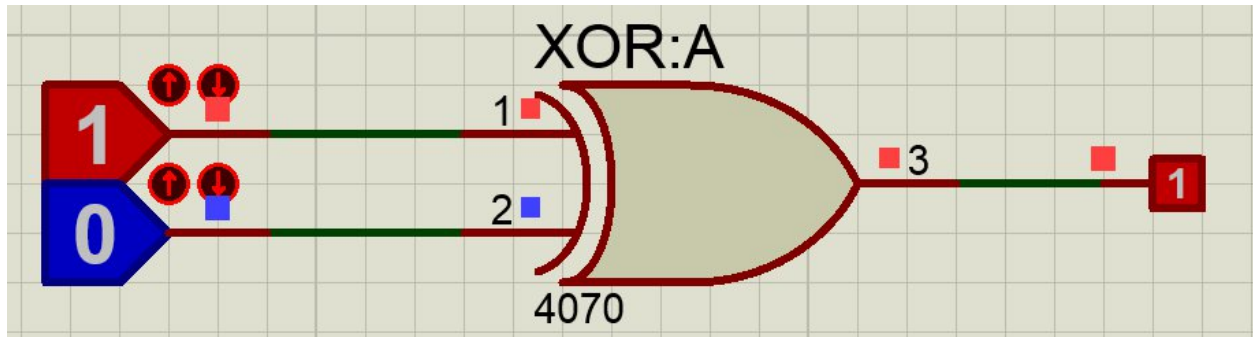

2-input XNOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

74266 and 4077 IC

