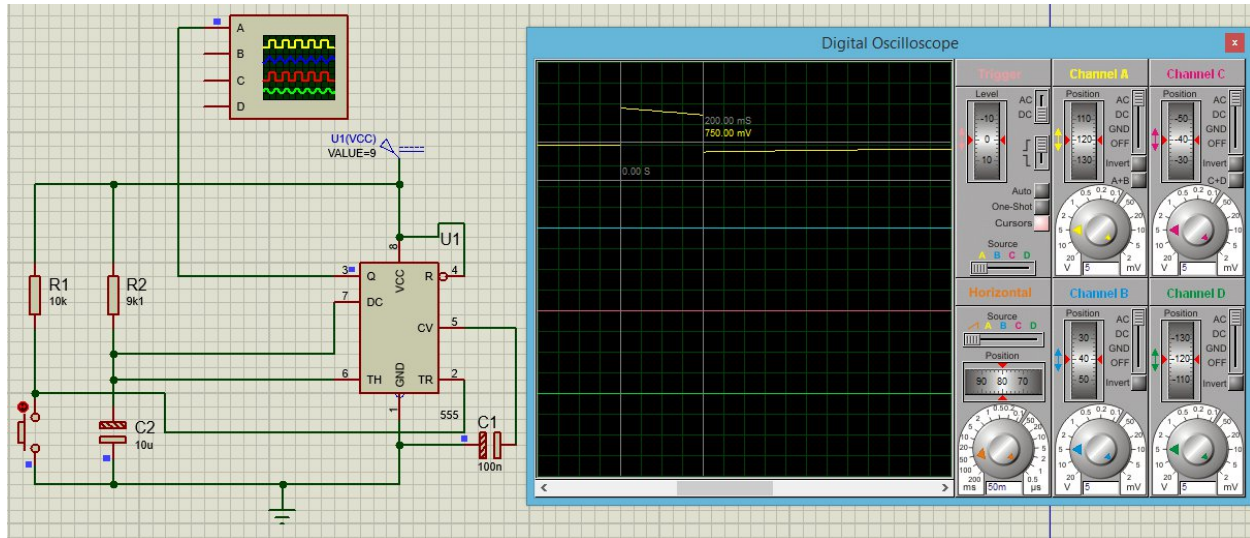


ME 2261 - Embedded Systems Log Book**Lab Practical 2****Task 1**

$$T = 1.1RC$$


$$= 1.1 \times 9.1 \text{ k}\Omega \times 10 \text{ uF}$$

$$= 100.1 \text{ ms}$$


Time period obtained in the Oscilloscope = 200 ms

Task 2

Series

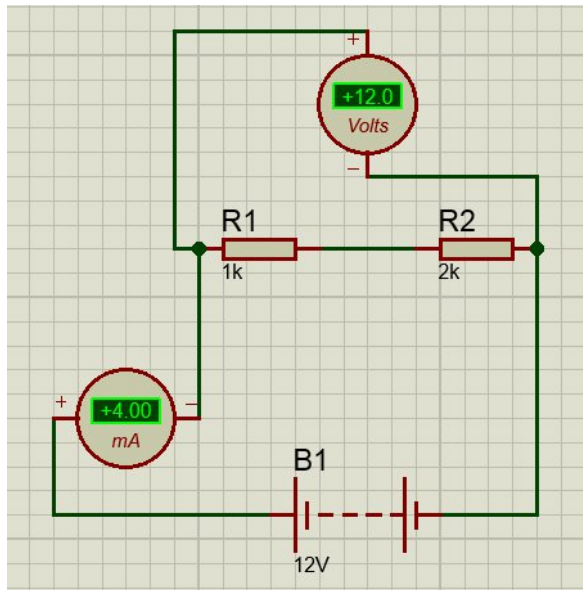

Parallel

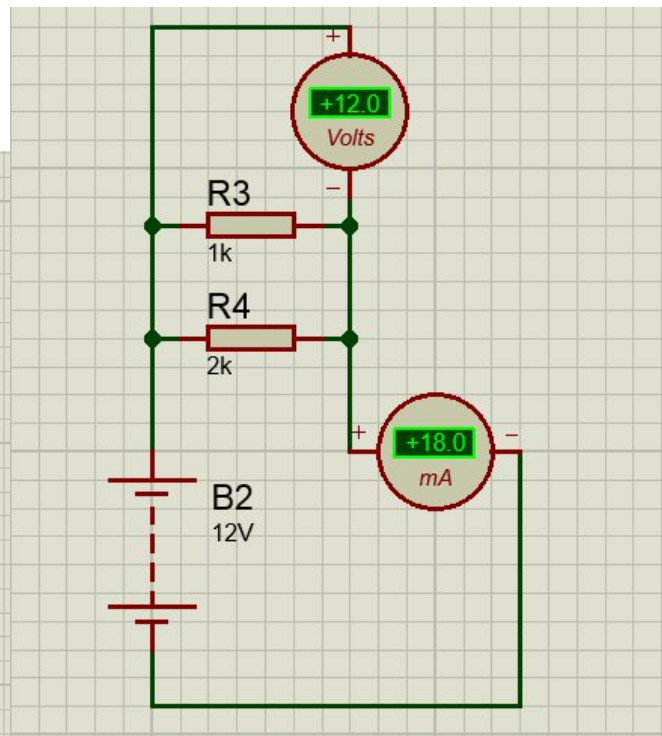



Total Resistance = V/I

In Series mode, $TR = 12/4 \times 10 = 3 \text{ k}\Omega$



In Parallel mode, $TR = 12/18 = 0.66 \text{ k}\Omega$

Task 3

Charging process

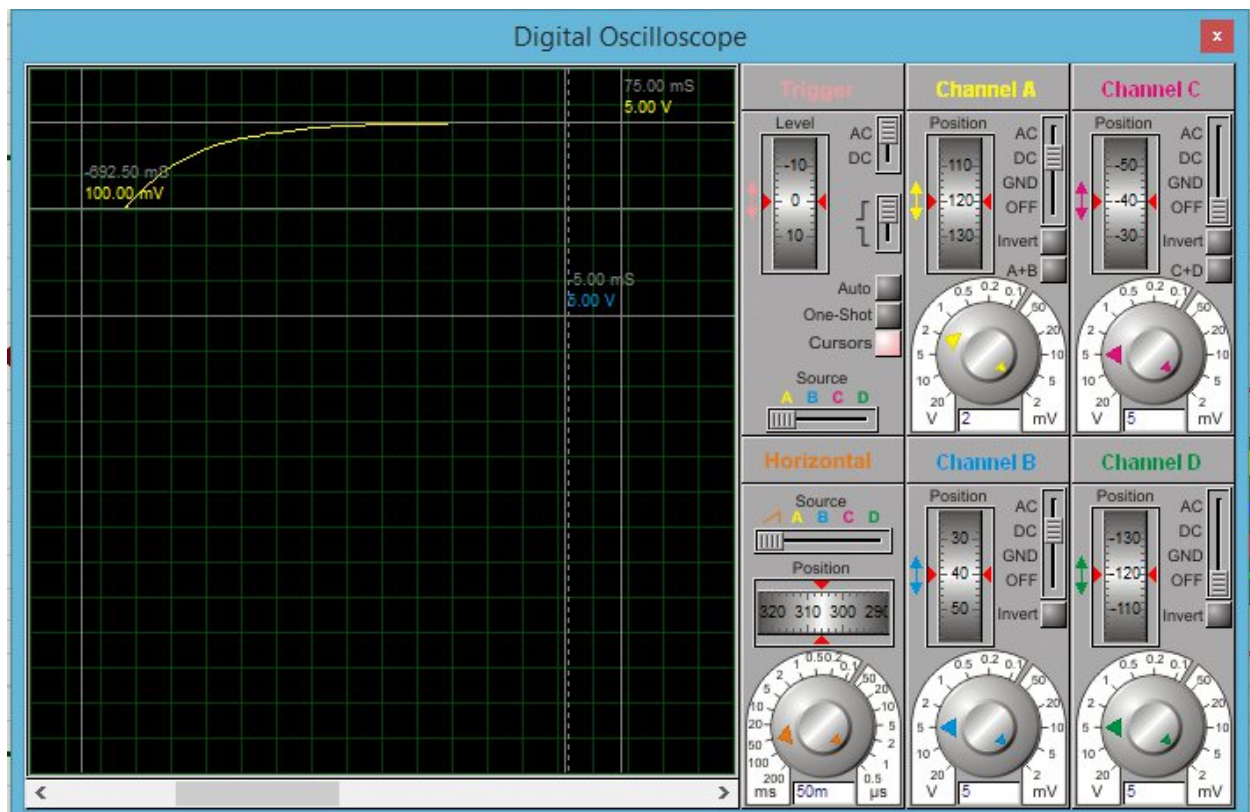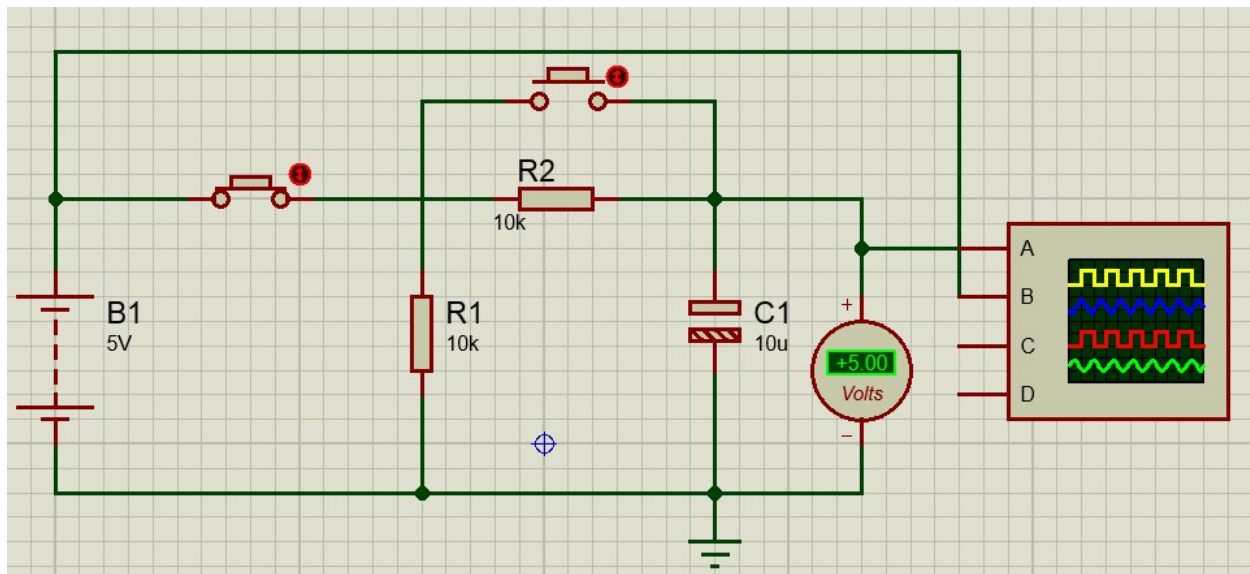

Discharging process

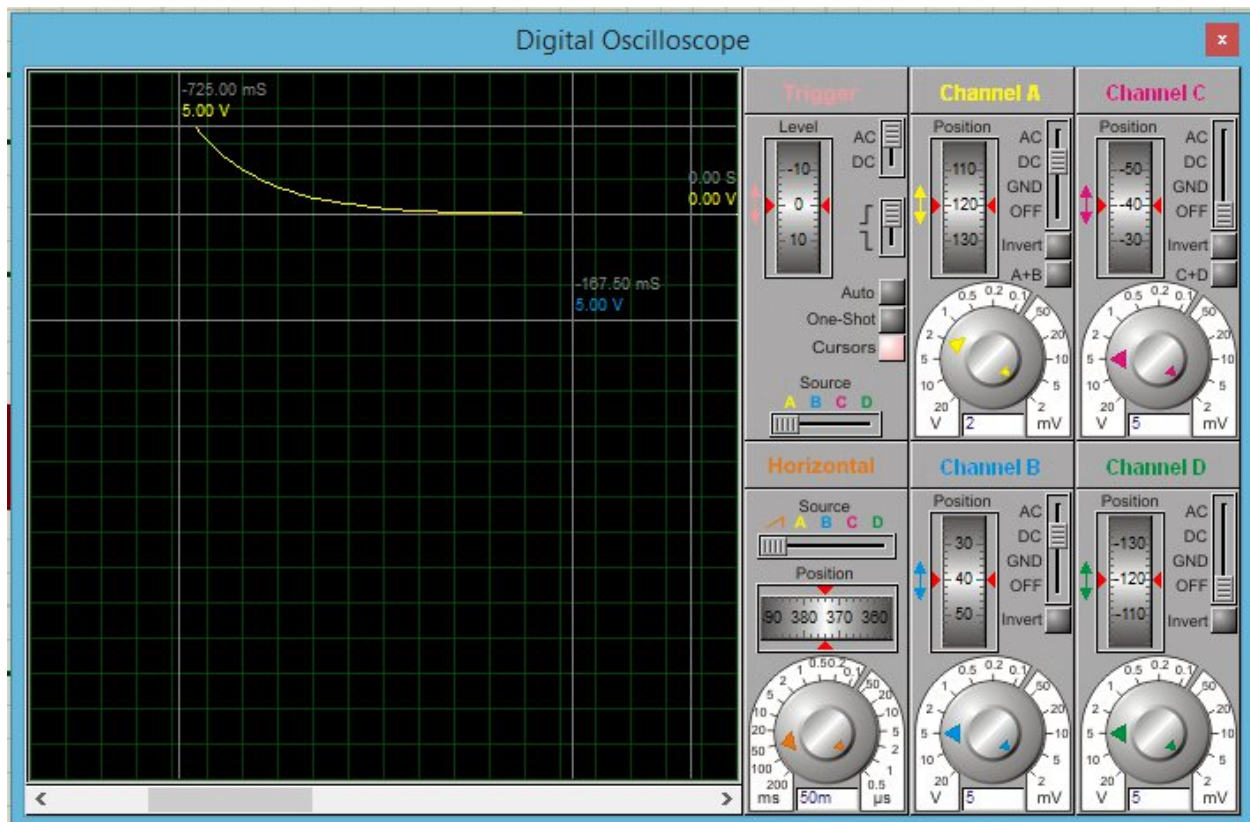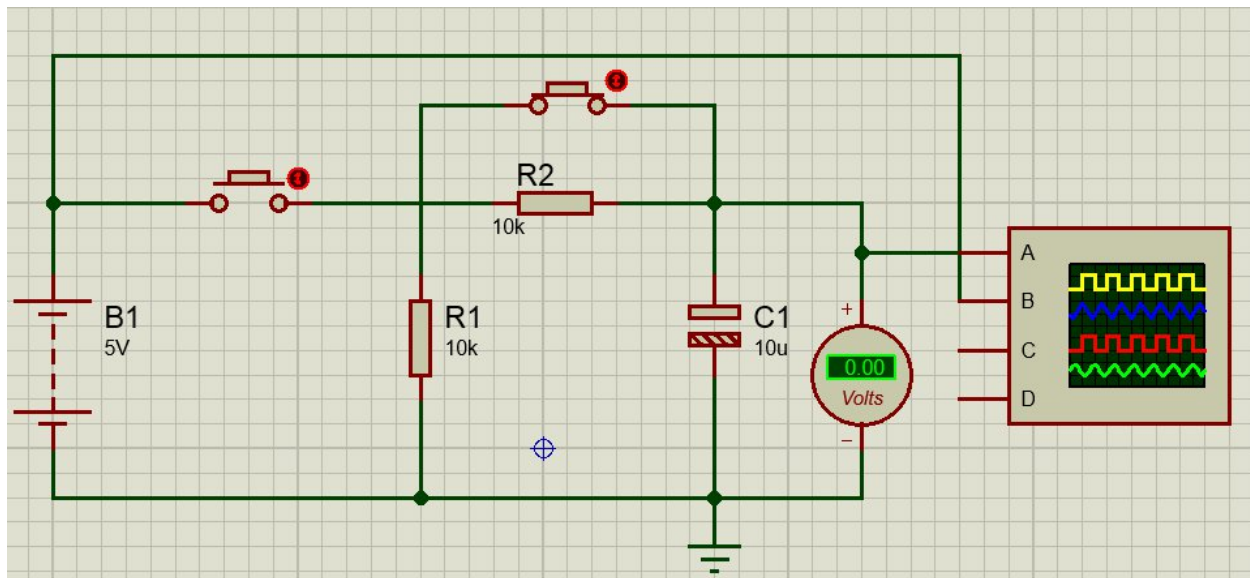


Task 4

Truth table


$$Y = (A \cdot B) + \bar{A}$$

A	B	$A \cdot B$	$\bar{A}$	$(A \cdot B) + \bar{A}$
0	0	0	1	1
0	1	0	1	1
1	0	0	0	0
1	1	1	0	1

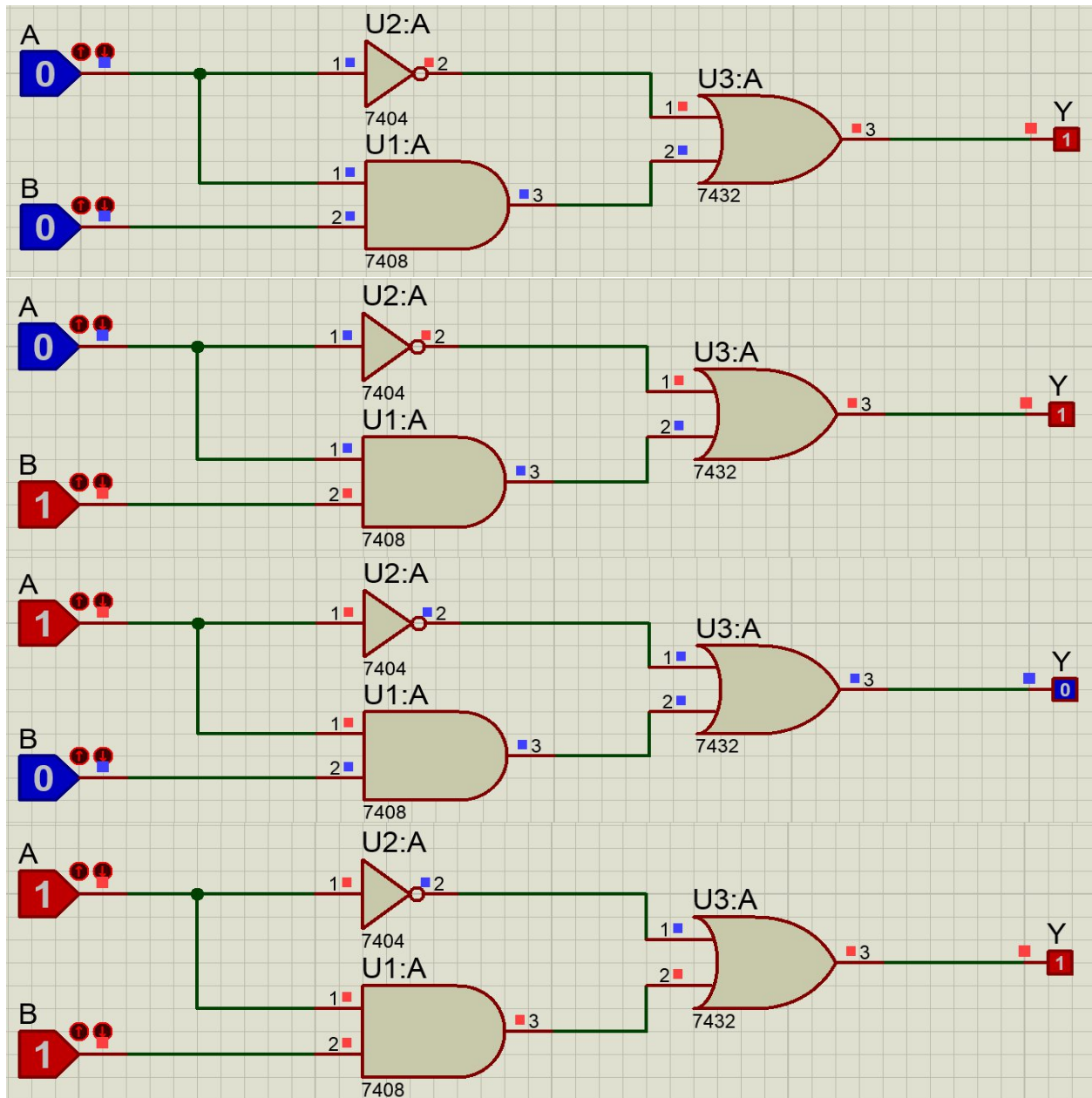

Task 5


Pull up Resistor

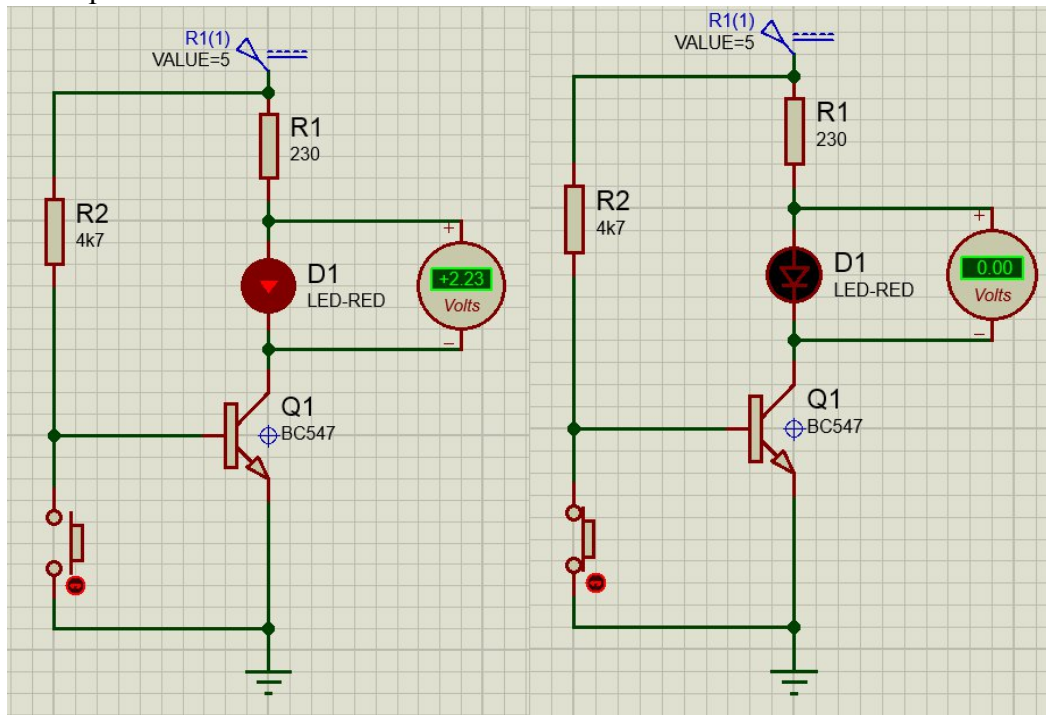

Input is LOW

Input is HIGH

Pull Down Resistor

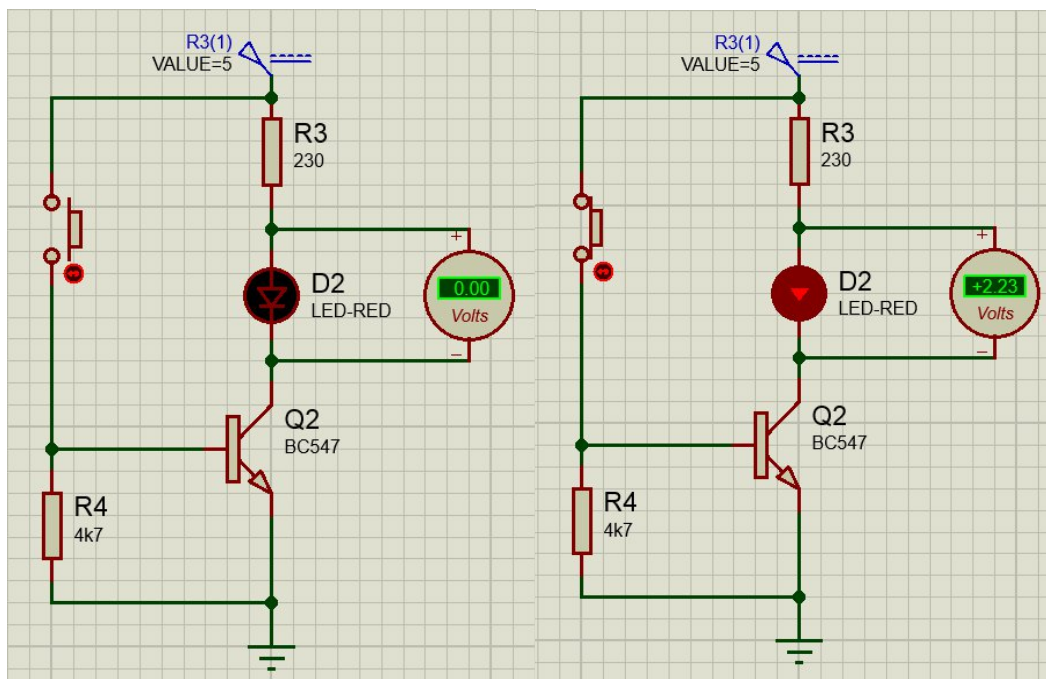

Input is LOW

Input is HIGH